

## Lecture 37, Apr 11, 2022

### Power In Terms of RMS Values

- Average power can be expressed in terms of the RMS voltage and current as  $P_{ave} = V_{rms}I_{rms} \cos(\theta_v - \theta_i)$ 
  - Using phasors  $P_{ave} = \text{Re}(\mathbf{V}_{rms}\mathbf{I}_{rms}^*)$
- Likewise for reactive power  $Q = V_{rms}I_{rms} \sin(\theta_v - \theta_i)$ 
  - Using phasors  $Q = \text{Im}(\mathbf{V}_{rms}\mathbf{I}_{rms}^*)$
- For an impedance, recall for  $\mathbf{Z} = R + jX$ , average power  $P_{ave} = \text{Re}\left(\frac{(R + jX)|\mathbf{I}|^2}{2}\right) = \frac{1}{2}RI_m^2 = RI_{rms}^2$
- For reactive power,  $Q = \text{Im}\left(\frac{(R + jX)|\mathbf{I}|^2}{2}\right) = \frac{1}{2}XI_m^2 = XI_{rms}^2$

### Apparent Power & Power Factor

- Active power  $P_{ave} = \frac{1}{2}V_mI_m \cos(\theta_v - \theta_i) = V_{rms}I_{rms} \cos(\theta_v - \theta_i)$ , can be divided into two terms, the *apparent power*  $S = \frac{1}{2}V_mI_m = V_{rms}I_{rms}$  (in volt-amps), and the *power factor*  $PF = \cos(\theta_v - \theta_i)$
- Consider an impedance  $\mathbf{Z}$  with voltage  $\mathbf{V}$  and current  $\mathbf{I}$ ,  $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{V_m}{I_m} \angle(\theta_v - \theta_i)$ 
  - Notice the power factor is the cosine of the angle of the impedance here  $PF = \cos(\angle\mathbf{Z})$
- The power factor does not uniquely determine the impedance, since cosine is an even function, so given only a power factor we don't know if the angle of the impedance is positive or negative
  - Define a power factor as *leading* if current leads voltage, i.e.  $\theta_v - \theta_i < 0$ , and *lagging* if current lags voltage, i.e.  $\theta_v - \theta_i > 0$
- For a resistor,  $\angle\mathbf{Z} = 0$  so the power factor is  $\cos(0) = 1$ , neither lagging nor leading
  - This is the only type of impedance to have a power factor of 1
- For an inductor,  $\angle\mathbf{Z} = 90^\circ$  so the power factor is  $\cos(90^\circ) = 0$ , and lagging since  $\angle\mathbf{Z} > 0$
- For a capacitor,  $\angle\mathbf{Z} = -90^\circ$  so the power factor is also 0, but this time leading
- For an RL circuit,  $\mathbf{Z} = R + j\omega L$  so  $0^\circ < \angle\mathbf{Z} < 90^\circ$  so the power factor is between 0 and 1 lagging
- For an RC circuit,  $\mathbf{Z} = R - \frac{j}{\omega C}$  and the power factor is between 0 and 1 leading
- For an RLC circuit,  $\mathbf{Z} = R + j\left(\omega L - \frac{1}{\omega C}\right)$  so the power factor is between 0 and 1, either leading or lagging, depending on the relative values of the inductance and capacitance